

simple EE problem


39

- consider an electrical circuit with resistors, which can be placed in


– series



– parallel

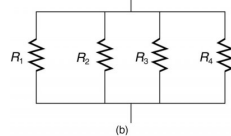

– combinations

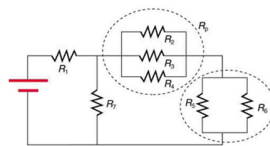

see: <https://courses.lumenlearning.com/physics/chapter/21-1-resistors-in-series-and-parallel/>


39

simple EE problem

40


- using Ohm's law any combination of resistors can be replaced by a **single equivalent resistor**

series:

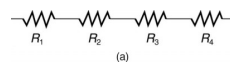

$$R_e = R_1 + R_2 + R_3 + R_4$$

parallel:

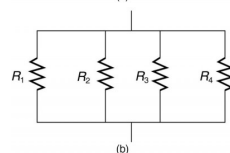


$$1/R_e = 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$

40

simple EE problem

41

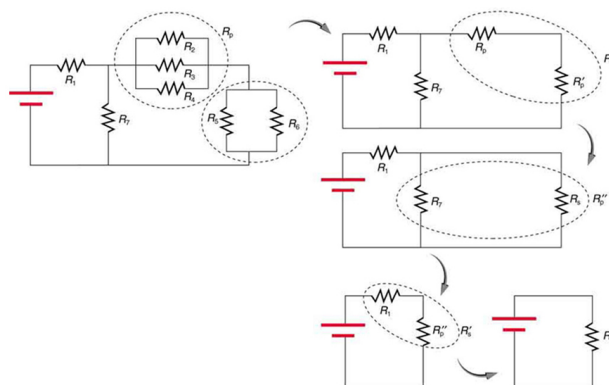- using Ohm's law any combination of resistors can be replaced by a [single equivalent resistor](#)




41

simple EE problem

42

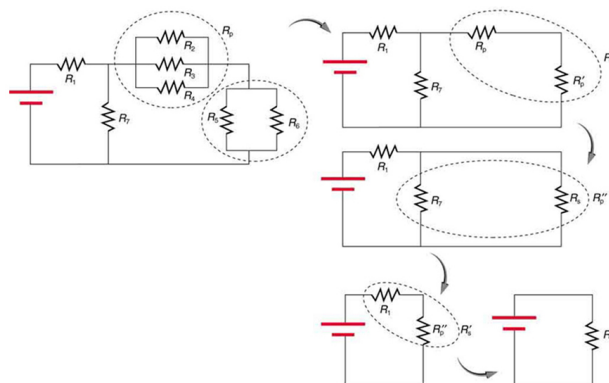- we will write a program that computes the equivalent resistance
- as we [add](#) resistors (the arrows are reversed)



42